

Gray Code

Used for mechanical shift encoders, etc. Its main property is that only one bit changes in going from one state to the next. This is a sort of error prevention strategy as we will see. This is especially useful when one cannot guarantee that all bit change simultaneously. Example in slides ...

Combinatorial vs Sequential Logic

Combinatorial

adding numbers
comparing numbers
parity check
convert binary to decimal

Output is pre-determined function of input.

Can be expressed by Boolean algebra and performed with gates.

Sequential

serial bits $\rightarrow$ parallel bits

counting the number of 1's in a sequence

giving an output every four input pulses

10110010

1
0
1
1
0
0
1
0

Output is based on the history of the input.


$\rightarrow$ Require digital memory implemented by flip-flops.

Example

2-Byte = 00000000 - FFFF, 2⁸ = 256
 4-Byte = 00000000 - FFFFFFFF, 2³² = 4294967296

Gates

OR

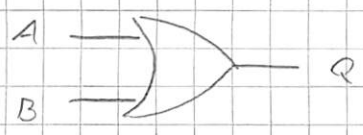

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

$A + B$, A OR B


AND



A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

$A \cdot B$, A AND B, AB

INVERT

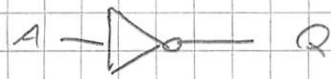

A	Q
0	1
1	0

$\bar{A}$, NOT A, A*

NAND



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

NOR



A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0


XOR



A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

Goto Interchangeability

3

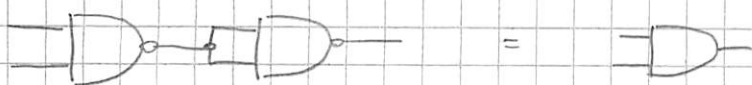

In general $\rightarrow$ multiple use of an inverting gate
(NAND or NOR) makes any function
 $\swarrow$ universal gates

De Morgan's Theorem

You can swap gates if you invert all inputs
& outputs:




0	0	0	T	T	T	1	1	1
0	1	0	T	F	T	1	0	1
1	0	0	F	T	T	0	1	1
1	1	1	F	F	F	0	0	0



How do gates work?

1960s version

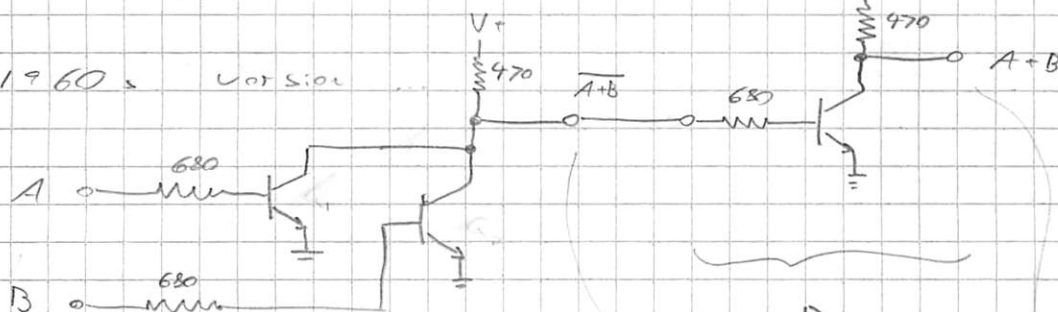


A	B	O
0	0	1
0	1	0
1	0	0
1	1	0

AB	O
00	0
01	1
10	1
11	1



slow!

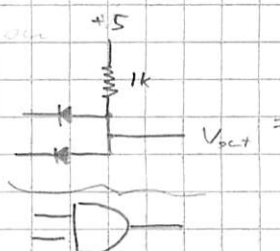

Combinatorial Logic

$$A \oplus B = \bar{A}B + A\bar{B}$$

w/ identities ...

$$A \oplus B = A\bar{A} + A\bar{B} + B\bar{A} + B\bar{B}$$

$$= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B})$$

$$= A(\overline{AB}) + B(\overline{AB})$$

(DeMorgan's Theorem)


$$A \oplus B = (A + B)(\overline{AB})$$

XOR

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


$\therefore$ XOR

$$\bar{A}B + A\bar{B}$$

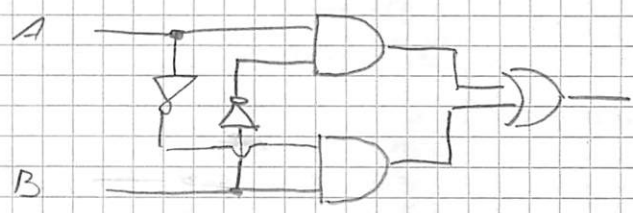

or

$$(A + B)(\overline{AB})$$






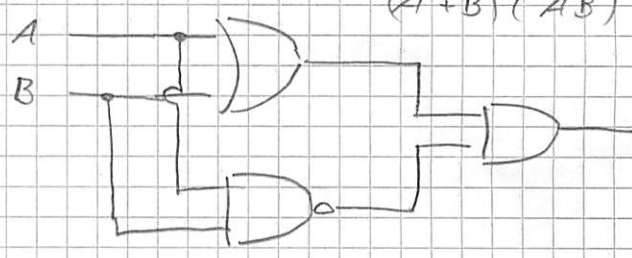


Karnaugh map slide ...

(Complementary Metal Oxide Semiconductor)

(5)


CMOS

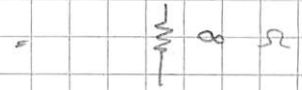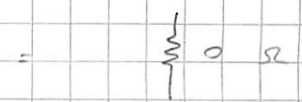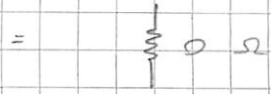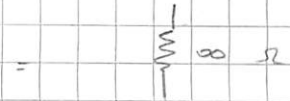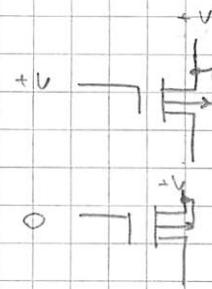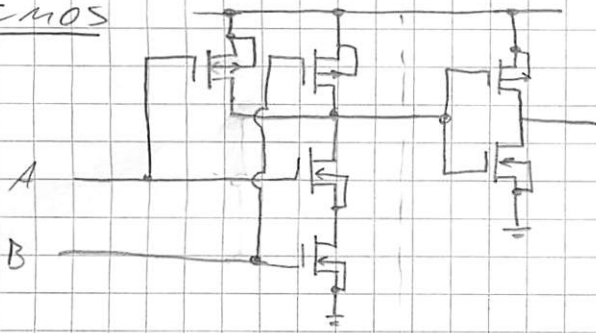


A	B	O
0	0	0
0	1	0
1	0	0
1	1	1

(Transistor-Transistor Logic)

TTL

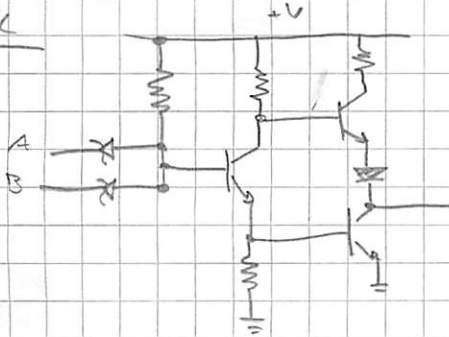


A	B	O
0	0	1
0	1	1
1	0	1
1	1	0

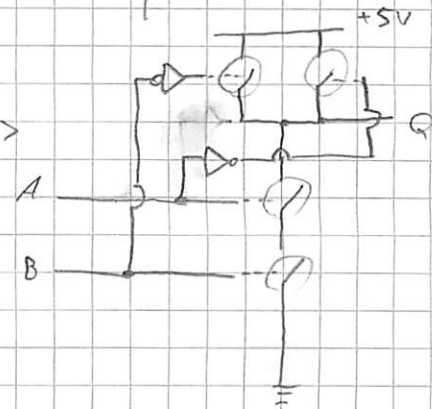


TTL Levels & Noise Margins

TTL

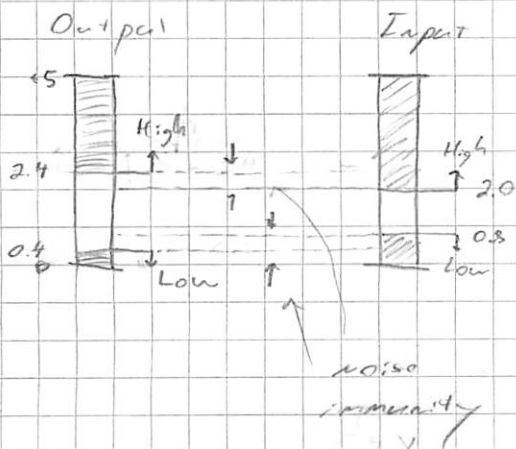



CMOS

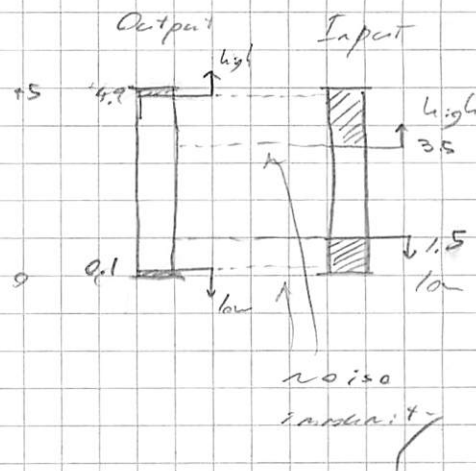



3-state Logic

6

Slow Slide

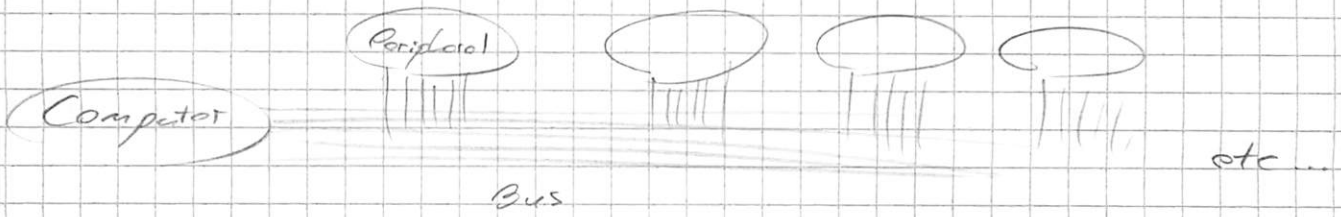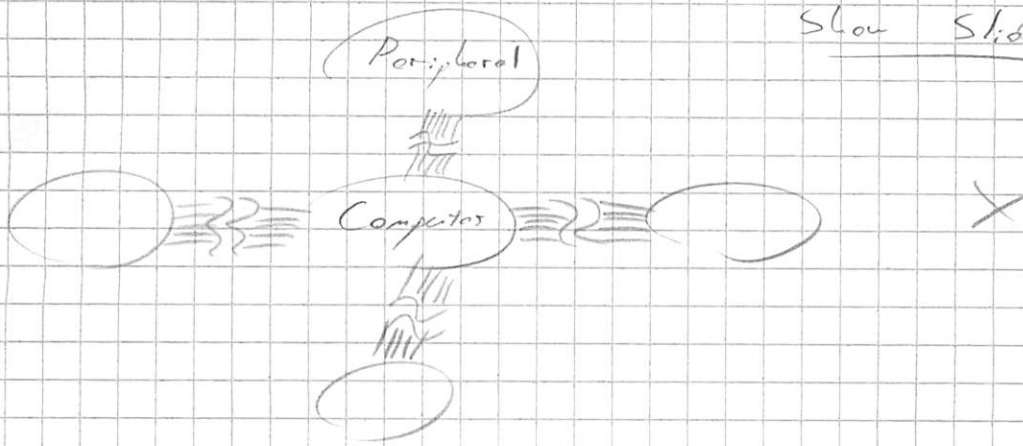

Requires Gates like this:

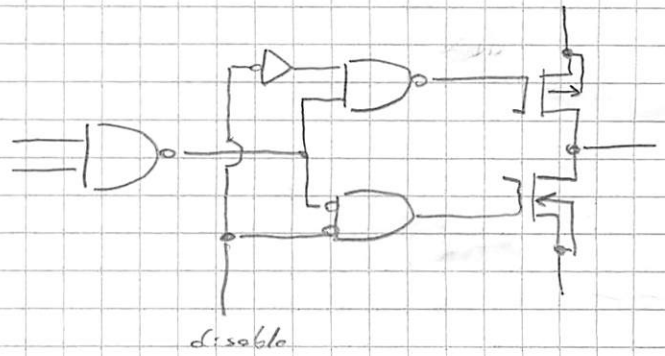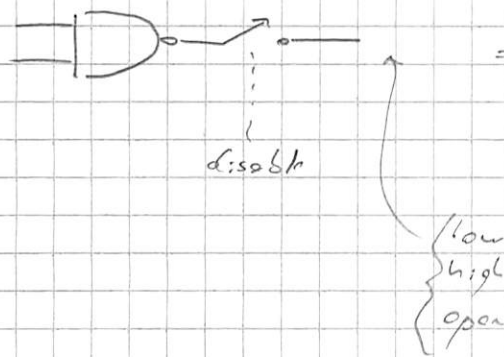

Multiplexers

For routing signals...

8-input MUX:

